

Roll No.

BCA-10 (Bachelor of Computer Application)

Second Semester Examination-2014

BCA-201

Basic Digital Electronics

Time Allowed : Three Hours

Maximum Marks : 60

**Note : The paper is divided into three sections A, B and C.
Notes for each section are given in the section itself.**

Section - A

(Long answer type Questions)

Note : Answer any 2 Question. Each question carries 15 marks. (2×15=30)

1. What are Flip-Flops ? Explain the types of Flip-Flops.
2. What are universal gate? Explain the operation of 2-input XOR gate and realize it using universal gate.
3. What are the differences between asynchronous and synchronous counter? Draw a MOD-8 counter and explain its working principle.

4. Draw the block diagram of a typical (2048 x 16) bits ROM and describes its working principles.

Section - B

(Short answer type Questions)

Note : Answer any 4 question. Each question carries 5 marks. (4×5=20)

1. Define and describe DeMorgan's Theorem.
2. Perform the following by 2's complement method:
 - a) 10101 - 11011
 - b) 100011 - 1111
3. Convert the following to its decimal equivalent:
 - a) $(81B6.F)_{16}$
 - b) $(765.45)_8$
4. Prove that (i) $x \cdot x = x$ (ii) $x + xy = x$
5. What is sequential circuit ? How it differ from combinational circuit?
6. Differentiate between RISC and CISC architecture.
7. What are the main component of CPU of a computer system ? Explain.
8. What is RAM? Give an example. Differentiate SRAM with DRAM.,

Section - C

(Objective type Questions)


Note : Answer all questions. Each question carries 1 Marks.

(10×1=10)

1. Which operations is called Modulo-2-Sum operations :

- (a) AND
- (b) OR
- (c) XOR
- (d) None of these

2. The following logic diagram

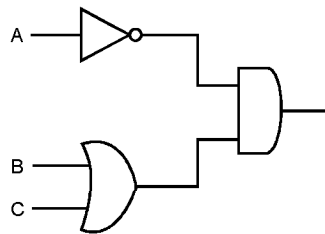

- (a) $D = A' \cdot (B+C)$
- (b) $D = A' \cdot (B+C)'$
- (c) $D = A' \cdot (B+AC)$
- (d) $D = A \cdot (B+C)$

3. Shift registers are

- (a) basically a sequential circuit
- (b) a combinational circuit
- (c) permanent memory
- (d) none of these

4. Magnitude comparator

- (a) magnify any digital signal
- (b) compares two multi bit binary number
- (c) compress binary numbers.
- (d) check error in a binary number

5. A 8-to-1 multiplexer has
(a) 1 control lines (a) 2 control lines
(c) 3 control lines (d) 4 control lines
6. A half-adder can add :
(a) Two binary bit
(b) Two binary number of 4 bit each
(c) Add half of a binary number
(d) None of these
7. The storage element of static device RAM is:
(a) Diode (b) Register
(c) Capacitor (d) Flip-flop
8. T flip-flop is commonly used as:
(a) a digital counter only
(b) a delay switch.
(c) a digital counter and frequency divider
(d) none of these
9. Binary number 1100 in gray code will be represented as
(a) 1010 (b) 1000
(c) 0011 (d) 1001
10. A 3-variable Karnaugh map has
(a) eight cells (b) three cells
(c) sixteen cells (d) four cells