

S-15

Roll No.

MCA–02/PGDCA–02/M.Sc. IT–02

Digital Logic

Master of Computer Application/P. G. Diploma in
Computer Application/Master of Science in
Information Technology
(MCA/PGDCA/M.Sc. IT-11/12/16/17)

First Semester, Examination, 2018

Time : 3 Hours

Max. Marks : 80

Note : This paper is of **eighty (80)** marks containing **three (03)** Sections A, B and C. Learners are required to attempt the questions contained in these sections according to the detailed instructions given therein.

Section–A

(Long Answer Type Questions)

Note : Section ‘A’ contains four (04) long answer type questions of nineteen (19) marks each. Learners are required to answer *two* (02) questions only.

1. What are Universal gate ? Explain the operations of 2-input XNOR gate and realize it using NOR gates.
2. What are the differences between asynchronous and synchronous counter ? Draw a MODE-8 counter and explain its working principle.

A-19 **P. T. O.**

3. What is memory ? Explain various types of memories in digital system. List the advantages and limitations of magnetic disk and magnetic tapes as a secondary storage device.
4. What is RAM ? Differentiate SRAM with DRAM. A memory chip is organized as (1024×4) bits RAM. Find the number of such chips required to obtain :
 - (a) (2048×8) RAM
 - (b) 4k bytes of RAM

Section–B

(Short Answer Type Questions)

Note : Section ‘B’ contains eight (08) short answer type questions of eight (8) marks each. Learners are required to answer *four* (04) questions only.

1. Find decimal equivalent of :
 - (i) $(53A.0B4)_{16}$
 - (ii) $(123.21)_8$
2. Convert the following Gray codes to Binary codes :
 - (i) 11011
 - (ii) 100111
3. Explain Maxterm and Minterm.
4. Define and describe De-Morgan’s Theorem.
5. With truth table and logic diagram, explain the working of a full adder circuit.
6. Explain the principle of an encoder and decoder.
7. What are sequential circuits ? Distinguish between combinational circuit and sequential circuit.

[3]

S-15

8. Differentiate between RISC and CISC architecture. Explain ROM family. Discuss the applications of ROM.

Section–C

(Objective Type Questions)


Note : Section ‘C’ contains ten (10) objective type questions of one (01) mark each. All the questions of this section are compulsory.

1. The ASCII is a standard bits code.
 - (a) 7
 - (b) 6
 - (c) 8
 - (d) 4
2. Radix of binary number system is
 - (a) 3
 - (b) 4
 - (c) 6
 - (d) 2
3. Which one of the following is not a valid rule of Boolean algebra ?
 - (a) $A + 1 = 1$
 - (b) $A = A'$
 - (c) $A . A = A$
 - (d) $A . 1 = A$

4. According to the associative law of addition :

- (a) $AB = BA$
- (b) $A = A + A$
- (c) $A + (B + C) = (A + B) + C$
- (d) $A + B = B + A$

5. The following logic diagram :

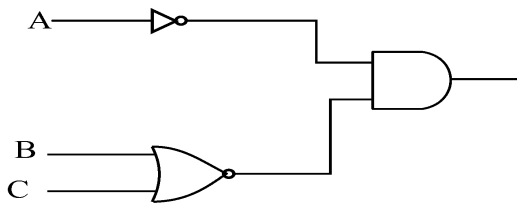

is represented by the function :

- (a) $D = A' \cdot (B + C)$
 - (b) $D = A' \cdot (B + C)'$
 - (c) $A' \cdot B + AC$
 - (d) $D = A \cdot (B + C)$
6. Shift register are :
- (a) basically a sequential circuit
 - (b) a combinational circuit
 - (c) permanent memory
 - (d) None of these
7. A 8-to-1 multiplexer has :
- (a) 1 control lines
 - (b) 2 control lines
 - (c) 3 control lines
 - (d) 4 control lines

[5]

S-15

8. A half-adder can add :
- (a) Two binary bit
 - (b) Two binary number of 4 bit each
 - (c) Add half of a binary number
 - (d) None of these
9. A simple flip-flop :
- (a) is 2 bit memory
 - (b) is 1 bit memory
 - (c) is a four state device
 - (d) has nothing to do with memory
10. Volatile memory device is :
- (a) ROM
 - (b) RAM
 - (c) Both of the above
 - (d) None of these

S-15

220

